

Technical Article

Factory 11, 30 Perry Street Matraville NSW Australia 2036 Ph. 61 2 9316 6909 Fax: 61 2 9316 6797 Email sales@ecd.com.au

Ref: Gong board article

Date: Jan 25th 2018


Gong Board P/N 100-125/4S, 8S, 12S

Description: The 100-125 range of gong boards are used to interface the controller to hall gong chimes and direction indicators. Gong boards are available in the following versions;

4 stop version. 100-125/4S. Dim. 90mm x 77mm 8 stop version. 100-125/8S. Dim. 125mm x 77mm 12 stop version. 100-125/12S. Dim. 160mm x 77mm

Mounting: For easy installation, all versions are mounted in a plastic housing, suitable for clipping on to 35mm DIN rail

Gong/Lantern

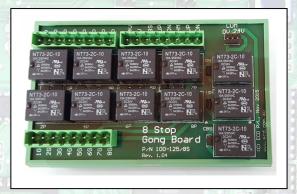

100-125/8S

Gong TOP/INTERMEDIATE Board and BOTTOM example. 100-125 0V CHM CBS CBS COM GUP 0v 24v DUF GDN J1 ••• DDN

DUP DDN 12P 12G 12P DN LANTERN 11P 11P 11G 10F 10G 10P to output 241 9P 9G 9P 8P 8G 8P UP LANTERN on 24V for position (1G-12G) and CHM switching to 0V 7P 7G 6G 6P 5P 5G DN LANTERN 5P

4G

2G

1G

links on GUP an

e: Put 1 GDN.

GUP

and

e: Put l GDN,

UP LANTERN

Wiring:

- The 100-125 board is supplied from a 24VDC supply. Wire 24VDC to the 24V and 0V terminals.
- Inputs 1P to 12P are wired to the 24VDC position outputs from controller.
- Input CBS is wired to the 24VDC CBS output from controller. This output turns on when answering hall calls to turn on the hall gong chimes and direction indicators.
- Input DUP is wired to the 24VDC up position output from controller.
- Input DDN is wired to the 24VDC down position output from controller.
- Outputs 1G to 12G are wired to the respective floor gongs/chimes and direction indicators.
- Output CHM is wired to all the floor gong/chime units.
- Input GUP is wired to all the up direction indicators.
- Input GDN is wired to all the down direction indicators.

Note: Put links on 0V for position (1G-12G) to output 0V and GDN, GUP and CHM switching to 24V

Note: Put links on 24V for position (1G-12G) to output 24V and GDN, GUP and CHM switching to 0V

Operation Example;

Figure 1

1P

4P

3P

2P

1P

Down gong and hall lantern on level 6 to operate as 6 down hall call is answered;

As elevator answers 6 down hall call (inputs in green), relays 6P, CBS and DN on the 100-125 board will be energized. This will result in 24VDC at terminal CHM and GDN. Terminal 6G will be at 0V.

As seen from the figure 1, 24v flows from terminal CHM through the chime on level 6 to 0V at terminal 6G. See red trace 24V also flows from terminal GDN through the DN Lantern on level 6 to 0V at terminal 6G. See blue trace. Nb: Links to be on 0V as per figure 1.